

# **Digital IC Design**

## **Final Team Project:**

### **32-Rows x 4-Columns Digital Computation-in-Memory Macro for Matrix Multiplications**

**Professor Po-Tsang Huang**

**International College of Semiconductor Technology  
National Yang Ming Chiao Tung University**



# Design a Digital CIM Macro

## ■ Spec of CIM macro:

### ◆ Array Size:


- 512bit
- 32rows x 4 columns x 4bit

### ◆ CIM cell:

- 6T SRAM + NOR (Provided by TA)
 
### ◆ Pre-store data:

- Weights should be stored in SRAM cells by initial conditions (.IC)



# Design a Digital CIM Macro

## ■ Spec of matrixes:

### ◆ Inputs matrix (unsigned values):

- 4 rows x 32 columns:  $(I_1, I_2, \dots, I_{32})_1, (I_1, I_2, \dots, I_{32})_2, \dots (I_1, I_2, \dots, I_{32})_4$
- All inputs are 4bit
- **Give the input bit serially:** 32 inputs (4 bits each) should be sent to the DCIM macro, 1 bit per cycle, over a total of 4 cycles to generate a column of output
- You can add any extra control signals for your design

### ◆ Weights matrix(unsigned values):

- 32 rows x 4 columns:  $(W_1, W_2, W_3, W_4)_1, (W_1, W_2, W_3, W_4)_2, \dots (W_1, W_2, W_3, W_4)_{32}$
- All weights are 4bit
- **Weights should be stored in latches by initial conditions (.IC)**

### ◆ Output matrix (unsigned values):

- 4 rows x 4 columns:  $(O_1, O_2, O_3, O_4)_1, (O_1, O_2, O_3, O_4)_2, \dots (O_1, O_2, O_3, O_4)_4,$
- All outputs are 13 bits
- $(O_1)_1 = ((I_1)_1 \times (W_1)_1) + ((I_2)_1 \times (W_1)_2) + \dots ((I_{32})_1 \times (W_1)_{32})$
- $(O_2)_1 = ((I_1)_1 \times (W_2)_1) + ((I_2)_1 \times (W_2)_2) + \dots ((I_{32})_1 \times (W_2)_{32})$
- $(O_1)_2 = ((I_1)_2 \times (W_1)_1) + ((I_2)_2 \times (W_1)_2) + \dots ((I_{32})_2 \times (W_1)_{32})$

# Design a Digital CIM Macro

## Input & Output ports

Input signal	Bit width	Definition
$I_1 - I_{32}$	1bit x 32	Input serial signals
Output signal	Bit width	Definition
Out_valid	1	$O_1 - O_4$ are valid
$O_1 - O_4$	13bit x 4	Output signals


\*You can add Control signals and define by yourself

## Matrixes:

$$\begin{bmatrix} (I_1)_1 & (I_2)_1 & \dots & (I_{32})_1 \\ (I_1)_2 & (I_2)_2 & \dots & (I_{32})_2 \\ \vdots & \vdots & \ddots & \vdots \\ (I_1)_4 & (I_2)_4 & \dots & (I_{32})_4 \end{bmatrix} \times \begin{bmatrix} (W_1)_1 & (W_2)_1 & \dots & (W_4)_1 \\ (W_1)_2 & (W_2)_2 & \dots & (W_4)_2 \\ \vdots & \vdots & \ddots & \vdots \\ (W_1)_{32} & (W_2)_{32} & \dots & (W_4)_{32} \end{bmatrix} = \begin{bmatrix} (O_1)_1 & (O_2)_1 & \dots & (O_4)_1 \\ (O_1)_2 & (O_2)_2 & \dots & (O_4)_2 \\ \vdots & \vdots & \ddots & \vdots \\ (O_1)_4 & (O_2)_4 & \dots & (O_4)_4 \end{bmatrix}$$

# Digital CIM Macro

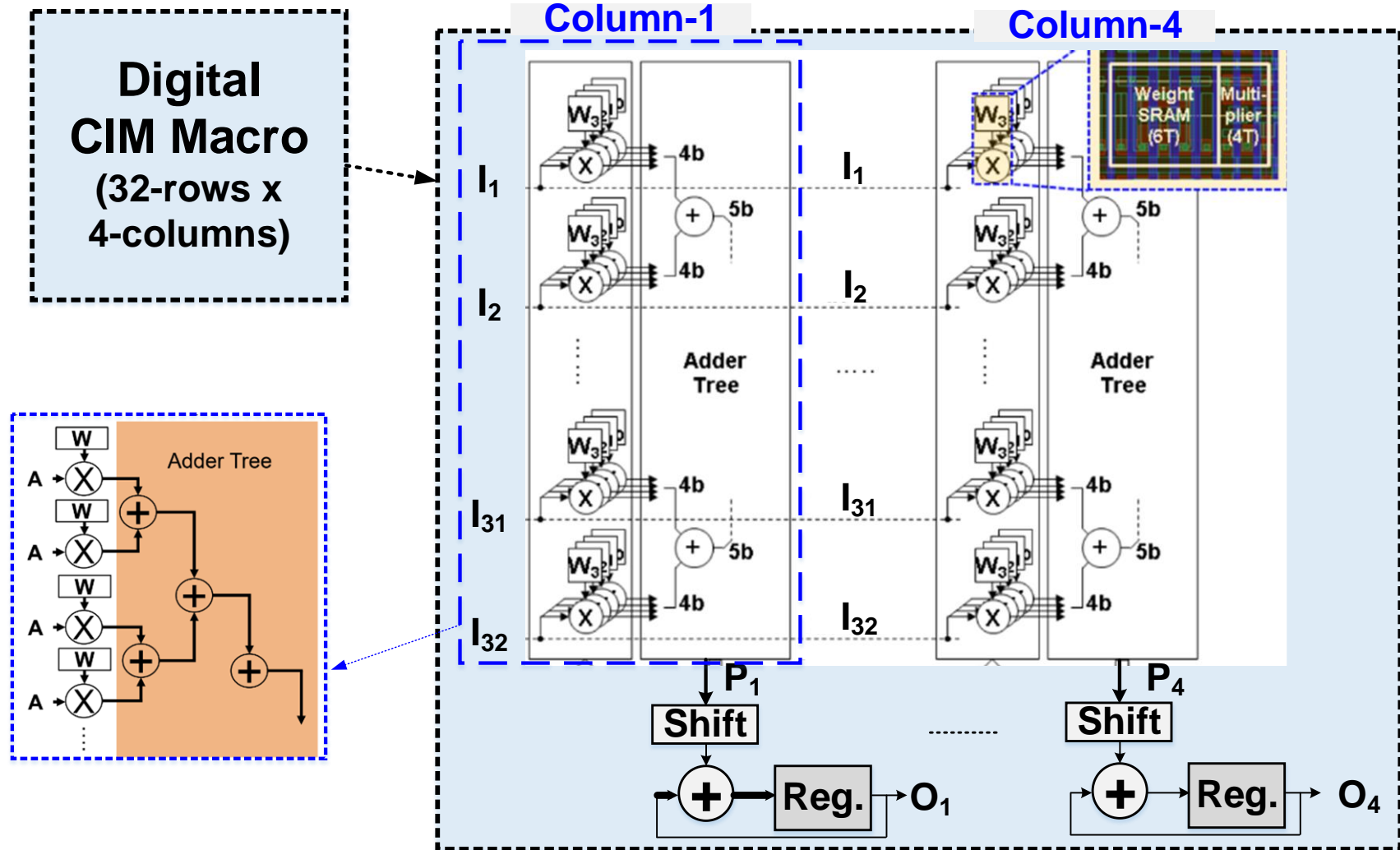
- Example of 32-rows x 4-columns DCIM macro



# Example of Bit Serial Input

## ■ Example of Waveform

### ◆ Bit Serial input

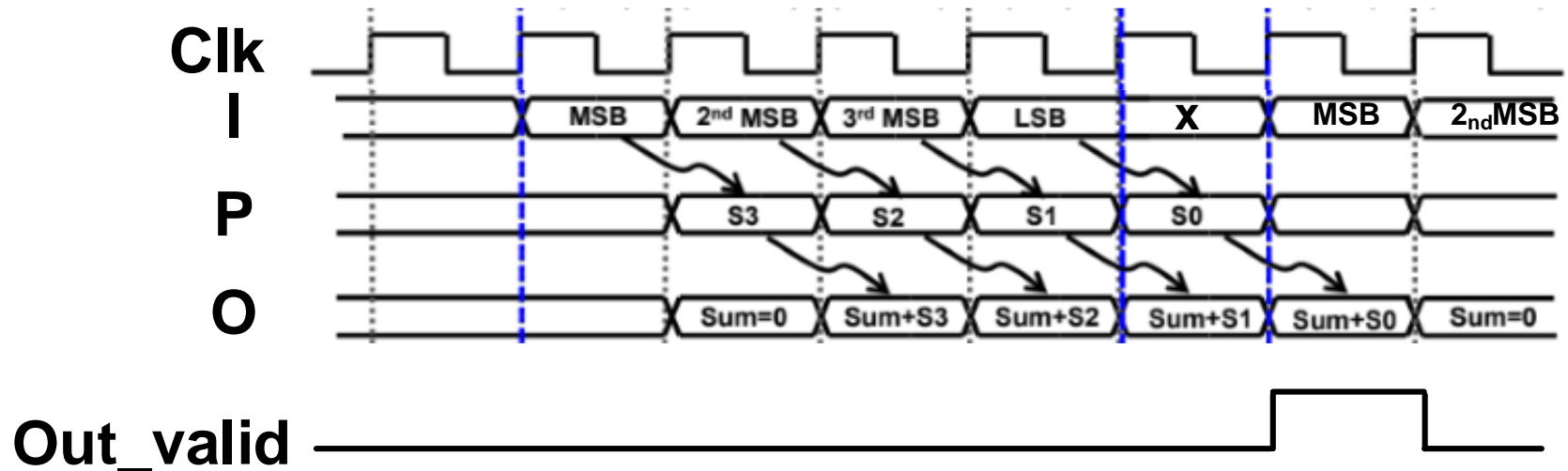

# Maximize the energy efficiency

---

- Maximize the energy efficiency **under 2 different throughput, respectively:**
  - ◆ When the **throughput** is higher than **30 GOPS**
  - ◆ When the **throughput** is higher than **80 GOPS**
  - ◆  $1\text{MAC} = 2\text{ OPs}$
- The Frequency and Voltage can be adjusted by yourself
- The input/weight matrixes should be random patterns
- The function should be correct
  - ◆ Provide correct waveform (Each Outputs should be combined into a bus signal(13bit) in Decimal format)
  - ◆ Example of 13bit bus signal in Decimal format :

